

Chapter 1

Boolean Logic

These slides support chapter 1 of the book

The Elements of Computing Systems

(1st and 2nd editions)

By Noam Nisan and Shimon Schocken

MIT Press

Chapter 1: Boolean logic

Theory

- Basic concepts
- Boolean algebra
- Boolean functions
- Nand

Practice

- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses

Project 1

- Introduction
- Chips
- Guidelines

Chapter 1: Boolean logic

Theory



Basic concepts

- Boolean algebra
- Boolean functions
- Nand

Practice

- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses

Project 1

- Introduction
- Chips
- Guidelines


Boolean values



Boolean values




Boolean values

 

off no false 0



on yes true 1

 

George Boole
1815 - 1864

- Boolean / binary *values*: 0, 1
- Boolean / binary *variable*: holds a 0, or a 1

Boolean values

b_0



1 binary variable: 2 possible states

Boolean values

b_1 b_0



1 binary variable: 2 possible states

2 binary variables: 4 possible states

Boolean values

b_2 b_1 b_0



1 binary variable: 2 possible states

2 binary variables: 4 possible states

3 binary variables: 8 possible states

Boolean values

\dots b_2 b_1 b_0



1 binary variable: 2 possible states

2 binary variables: 4 possible states

3 binary variables: 8 possible states

\dots

Boolean values

\dots b_2 b_1 b_0



1 binary variable: 2 possible states

2 binary variables: 4 possible states

3 binary variables: 8 possible states

\dots

Question: How many different states can be represented by N binary variables?

Boolean values

\dots b_2 b_1 b_0



1 binary variable: 2 possible states

2 binary variables: 4 possible states













3 binary variables: 8 possible states

\dots

Question: How many different states can be represented by N binary variables?

Answer: 2^N

Boolean functions


x	y	f
		
		
		
		

Boolean functions

x	y	f
0	0	0
0	1	0
1	0	0
1	1	1

Boolean functions

x	y	And
0	0	0
0	1	0
1	0	0
1	1	1

 

$$\text{And}(x,y) = \begin{cases} 1 & \text{when } x == 1 \text{ and } y == 1 \\ 0 & \text{otherwise} \end{cases}$$

Boolean function (like $\text{And}(x,y)$):

A function that operates on boolean variables, and returns a boolean value.

Boolean operator (like $x \text{ And } y$):

A simple boolean function that operates on a few boolean variables, called *operands*.

Boolean functions

x And y

x	y	And
0	0	0
0	1	0
1	0	0
1	1	1

x Or y

x	y	Or
0	0	0
0	1	1
1	0	1
1	1	1

Not(x)

x	Not
0	1
1	0

x Nand y

x	y	Nand
0	0	1
0	1	1
1	0	1
1	1	0

x Xor y

x	y	Xor
0	0	0
0	1	1
1	0	1
1	1	0

• • •

x f y

x	y	f
0	0	v_1
0	1	v_2
1	0	v_3
1	1	v_4

Boolean functions

x And y

x	y	And
0	0	0
0	1	0
1	0	0
1	1	1

x Or y

x	y	Or
0	0	0
0	1	1
1	0	1
1	1	1

Question:

How many Boolean functions $x f y$ exist over two binary (2-valued) variables?

Answer: 16

N binary variables span 2^{2^N} Boolean functions.

x Nand y

x	y	Nand
0	0	1
0	1	1
1	0	1
1	1	0

x Xor y

x	y	Xor
0	0	0
0	1	1
1	0	1
1	1	0

• • •

$x f y$

x	y	f
0	0	v_1
0	1	v_2
1	0	v_3
1	1	v_4

Boolean functions

x And y

x	y	And
0	0	0
0	1	0
1	0	0
1	1	1

x Or y

x	y	Or
0	0	0
0	1	1
1	0	1
1	1	1

Not(x)

y	Not
0	1
1	0

Boolean function evaluation (example):

Not(x Or (y And z))

Evaluate this function for, say,
 $x = 0, y = 1, z = 1$

Not(0 Or (1 And 1)) =

Not(0 Or 1) =

Not(1) =

0

Chapter 1: Boolean logic

Theory



Basic concepts



Boolean algebra

- Boolean functions
- Nand

Practice

- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses

Project 1

- Introduction
- Chips
- Guidelines

Some Boolean identities

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Some Boolean identities

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$

$\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

All these identities can be easily proved from the function definitions of And, Or, Not

For example, let's prove this identity

Boolean algebra

Prove

$$\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$$

$$f(x,y) = \text{Not}(x \text{ And } y)$$

x	y	f
0	0	
0	1	
1	0	
1	1	

$$g(x,y) = \text{Not}(x) \text{ Or } \text{Not}(y)$$

x	y	g
0	0	
0	1	
1	0	
1	1	

Proof: Fill in the right column in both truth tables.

If $f = g$, the identity is proved.

Boolean algebra

Prove

$$\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$$

$$f(x,y) = \text{Not}(x \text{ And } y)$$

x	y	f
0	0	1
0	1	1
1	0	1
1	1	0

$$g(x,y) = \text{Not}(x) \text{ Or } \text{Not}(y)$$

x	y	g
0	0	1
0	1	1
1	0	1
1	1	0

Proof: Fill in the right column in both truth tables.

If $f = g$, the identity is proved.

Boolean algebra

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation:

$$\boxed{\text{Not}(\text{Not}(x)) = x}$$



Substitution:

In any such identity, x and y can be substituted with any boolean function

Substitution examples:

$$\text{Not}(\text{Not}(a)) = a$$

$$\text{Not}(\text{Not}(u \text{ Or } v)) = u \text{ Or } v$$

Etc.

Boolean algebra

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Boolean algebra

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Task: Simplify this function (example):

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y))$



Boolean algebra

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Task: Simplify this function (example):

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y)) =$

By De Morgan's rule:

$\text{Not}(\text{Not}(x) \text{ And } (\text{Not}(x) \text{ And } \text{Not}(y)))$



Boolean algebra

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Task: Simplify this function (example):

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y)) =$

By De Morgan's rule:

$\text{Not}(\text{Not}(x) \text{ And } (\text{Not}(x) \text{ And } \text{Not}(y))) =$

By the associative rule:

$\text{Not}((\text{Not}(x) \text{ And } \text{Not}(x)) \text{ And } \text{Not}(y)) =$



Boolean algebra

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Task: Simplify this function (example):

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y)) =$

By De Morgan's rule:

$\text{Not}(\text{Not}(x) \text{ And } (\text{Not}(x) \text{ And } \text{Not}(y))) =$

By the associative rule:

$\text{Not}((\text{Not}(x) \text{ And } \text{Not}(x)) \text{ And } \text{Not}(y)) =$

By the idempotent rule:

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(y))$



Boolean algebra

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Task: Simplify this function (example):

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y)) =$

By De Morgan's rule:

$\text{Not}(\text{Not}(x) \text{ And } (\text{Not}(x) \text{ And } \text{Not}(y))) =$

By the associative rule:

$\text{Not}((\text{Not}(x) \text{ And } \text{Not}(x)) \text{ And } \text{Not}(y)) =$

By the idempotent rule:

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(y)) =$

By De Morgan's rule:

$\text{Not}(\text{Not}(x \text{ Or } y))$



Boolean algebra

Commutative: $x \text{ And } y = y \text{ And } x$
 $x \text{ Or } y = y \text{ Or } x$

Associative: $x \text{ And } (y \text{ And } z) = (x \text{ And } y) \text{ And } z$
 $x \text{ Or } (y \text{ Or } z) = (x \text{ Or } y) \text{ Or } z$

Distributive: $x \text{ And } (y \text{ Or } z) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $x \text{ Or } (y \text{ And } z) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $x \text{ And } x = x$
 $x \text{ Or } x = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Task: Simplify this function (example):

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y)) =$

By De Morgan's rule:

$\text{Not}(\text{Not}(x) \text{ And } (\text{Not}(x) \text{ And } \text{Not}(y))) =$

By the associative rule:

$\text{Not}((\text{Not}(x) \text{ And } \text{Not}(x)) \text{ And } \text{Not}(y)) =$

By the idempotent rule:

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(y)) =$

By De Morgan's rule:

$\text{Not}(\text{Not}(x \text{ Or } y)) =$

By double negation:

$x \text{ Or } y$

Boolean algebra

Observations about simplifying Boolean functions:

- Can lead to significant optimization
- Based on intuition, experience, and luck
- Can be assisted by some tools
- But, in general: *NP*-hard.

Task: Simplify this function (example):

$$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y)) =$$

By De Morgan's rule:

$$\text{Not}(\text{Not}(x) \text{ And } (\text{Not}(x) \text{ And } \text{Not}(y))) =$$

By the associative rule:

$$\text{Not}((\text{Not}(x) \text{ And } \text{Not}(x)) \text{ And } \text{Not}(y)) =$$

By the idempotent rule:

$$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(y)) =$$

By De Morgan's rule:

$$\text{Not}(\text{Not}(x \text{ Or } y)) =$$

By double negation:

$$x \text{ Or } y$$

Boolean algebra

Commutative: $(x \text{ And } y) = (y \text{ And } x)$
 $(x \text{ Or } y) = (y \text{ Or } x)$

Associative: $(x \text{ And } (y \text{ And } z)) = ((x \text{ And } y) \text{ And } z)$
 $(x \text{ Or } (y \text{ Or } z)) = ((x \text{ Or } y) \text{ Or } z)$

Distributive: $(x \text{ And } (y \text{ Or } z)) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $(x \text{ Or } (y \text{ And } z)) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $(x \text{ And } x) = x$
 $(x \text{ Or } x) = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Another example: Prove that

$x \text{ Or } y = \text{Not}(\text{Not}(x) \text{ And } \text{Not}(y))$

Boolean algebra

Commutative: $(x \text{ And } y) = (y \text{ And } x)$
 $(x \text{ Or } y) = (y \text{ Or } x)$

Associative: $(x \text{ And } (y \text{ And } z)) = ((x \text{ And } y) \text{ And } z)$
 $(x \text{ Or } (y \text{ Or } z)) = ((x \text{ Or } y) \text{ Or } z)$

Distributive: $(x \text{ And } (y \text{ Or } z)) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 $(x \text{ Or } (y \text{ And } z)) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$

De Morgan: $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Idempotent: $(x \text{ And } x) = x$
 $(x \text{ Or } x) = x$

Double negation: $\text{Not}(\text{Not}(x)) = x$

Another example: Prove that

$x \text{ Or } y = \text{Not}(\text{Not}(x) \text{ And } \text{Not}(y))$

De Morgan:

$\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$

Negate both sides:

$\text{Not}(\text{Not}(x \text{ Or } y)) = \text{Not}(\text{Not}(x) \text{ And } \text{Not}(y))$

By double negation:

$x \text{ Or } y = \text{Not}(\text{Not}(x) \text{ And } \text{Not}(y))$

Implication

- We don't really "need" Or
- We will soon revisit this reduction

Chapter 1: Boolean logic


Theory



Basic concepts



Boolean algebra

 

Boolean functions

- Nand

Practice

- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses

Project 1

- Introduction
- Chips
- Guidelines

Boolean function

Formula (example)

$$f(x, y, z) = (x \text{ And } (\text{Not}(y) \text{ Or } z)) \text{ And } y$$

Truth table

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

A Boolean function can be expressed using a *formula*, or a *truth table*

The two representations are equivalent

Question: Can we construct each representation from the other one?

Formula → truth table

Formula

$$f(x, y, z) = (x \text{ And } (\text{Not}(y) \text{ Or } z)) \text{ And } y$$



Truth table

x	y	z	f
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Formula → truth table

Formula

$$f(x, y, z) = (x \text{ And } (\text{Not}(y) \text{ Or } z)) \text{ And } y$$



Truth table

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	
0	1	1	
1	0	0	0
1	0	1	0
1	1	0	
1	1	1	

When $y = 0$, f must be 0

Formula → truth table

Formula

$$f(x, y, z) = (x \text{ And } (\text{Not}(y) \text{ Or } z)) \text{ And } y$$



Truth table

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	
1	1	1	

When $y = 0$, f must be 0

When $x = 0$, f must be 0

Formula → truth table

Formula

$$f(x, y, z) = (x \text{ And } (\text{Not}(y) \text{ Or } z)) \text{ And } y$$



Truth table

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

When $y = 0$, f must be 0

When $x = 0$, f must be 0

$(1 \text{ And } (\text{Not}(1) \text{ Or } 0)) \text{ And } 1 = 1$

$(1 \text{ And } (\text{Not}(1) \text{ Or } 1)) \text{ And } 1 = 1$

Formula ➡ truth table

Formula

$$f(x, y, z) = (x \text{ And } (\text{Not}(y) \text{ Or } z)) \text{ And } y$$



Truth table

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Lemma

Given a Boolean function expressed as a formula, we can always construct from it its truth table.

Proof: Evaluate the function over all the possible values of its variables (which is *the* definition of a truth table)

Boolean function synthesis: Truth table formula

Formula

$$f(x, y, z) = (x \text{ And } (\text{Not}(y) \text{ Or } z)) \text{ And } y$$



Truth table

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Can we also go the other way around,
for any given truth table?

Boolean function synthesis: Truth table \rightarrow formula

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Goal: Synthesize a formula which is equivalent to this truth table

Boolean function synthesis



x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

1. Focus on the rows where $f = 1$

Boolean function synthesis

x	y	z	f	f_1
0	0	0	1	1
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

Not(x) And Not(y) And Not(z)

1. Focus on the rows where $f = 1$
2. For each such row i , define a function f_i which equals 1 in row i and 0 elsewhere. Define f_i to be a conjunction of all of f 's variables or their negations, as the variable is 1 or 0 in the i 'th row

Boolean function synthesis

x	y	z	f	f_1	f_3
0	0	0	1	1	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	0

Not(x) And Not(y) And Not(z)

Not(x) And y And Not(z)

1. Focus on the rows where $f = 1$
2. For each such row i , define a function f_i which equals 1 in row i and 0 elsewhere. Define f_i to be a conjunction of all of f 's variables or their negations, as the variable is 1 or 0 in the i 'th row

Boolean function synthesis

x	y	z	f	f_1	f_3	f_5	
0	0	0	1	1	0	0	$\text{Not}(x) \text{ And } \text{Not}(y) \text{ And } \text{Not}(z)$
0	0	1	0	0	0	0	
0	1	0	1	0	1	0	$\text{Not}(x) \text{ And } y \text{ And } \text{Not}(z)$
0	1	1	0	0	0	0	
1	0	0	1	0	0	1	$x \text{ And } \text{Not}(y) \text{ And } \text{Not}(z)$
1	0	1	0	0	0	0	
1	1	0	0	0	0	0	
1	1	1	0	0	0	0	

1. Focus on the rows where $f = 1$
2. For each such row i , define a function f_i which equals 1 in row i and 0 elsewhere. Define f_i to be a conjunction of all of f 's variables or their negations, as the variable is 1 or 0 in the i 'th row

Boolean function synthesis

x	y	z	f	f_1	f_3	f_5	
0	0	0	1	1	0	0	$(\text{Not}(x) \text{ And } \text{Not}(y) \text{ And } \text{Not}(z))$ Or
0	0	1	0	0	0	0	
0	1	0	1	0	1	0	$(\text{Not}(x) \text{ And } y \text{ And } \text{Not}(z))$ Or
0	1	1	0	0	0	0	
1	0	0	1	0	0	1	$(x \text{ And } \text{Not}(y) \text{ And } \text{Not}(z))$
1	0	1	0	0	0	0	
1	1	0	0	0	0	0	
1	1	1	0	0	0	0	

1. Focus on the rows where $f = 1$
2. For each such row i , define a function f_i which equals 1 in row i and 0 elsewhere. Define f_i to be a conjunction of all of f 's variables or their negations, as the variable is 1 or 0 in the i 'th row
3. Define f to be the disjunction of all these conjunctions

Boolean function synthesis

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$(\text{Not}(x) \text{ And } \text{Not}(y) \text{ And } \text{Not}(z))$ Or

$(\text{Not}(x) \text{ And } y \text{ And } \text{Not}(z))$ Or

$(x \text{ And } \text{Not}(y) \text{ And } \text{Not}(z))$

Or

Disjunctive
Normal
Form (DNF)

$\text{Not}(z) \text{ And } (\text{Not}(x) \text{ Or } \text{Not}(y))$

(following
simplification)

1. Focus on the rows where $f = 1$
2. For each such row i , define a function f_i which equals 1 in row i and 0 elsewhere.
Define f_i to be a conjunction of all of f 's variables or their negations, as the variable is 1 or 0 in the i 'th row
3. Define f to be the disjunction of all these conjunctions

Boolean function synthesis

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Lemma

Given a boolean function expressed as a truth table, we can always synthesize a formula that expresses that function

Proof: Use the truth table to construct the DNF (which is a formula)

Theorem

Any boolean function can be represented as a formula containing only the operators And, Or, Not

Proof: Construct the function's truth table, then use the truth table to construct the DNF (which, by definition, uses only And, Or, Not).

Chapter 1: Boolean logic

Theory




Basic concepts



Boolean algebra



Boolean functions

 

Nand

Practice

- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses

Project 1

- Introduction
- Chips
- Guidelines

The expressive power of Nand

$x \text{ Nand } y$			$x \text{ And } y$			$x \text{ Or } y$			$\text{Not}(x)$	
x	y	Nand	x	y	And	x	y	Or	x	Not
0	0	1	0	0	0	0	0	0	0	1
0	1	1	0	1	0	0	1	1	1	0
1	0	1	1	0	0	1	0	1	0	1
1	1	0	1	1	1	1	1	1	1	0

Observations

- $\text{Not}(x) = x \text{ Nand } x$
- $x \text{ And } y = \text{Not}(x \text{ Nand } y)$
- $x \text{ Or } y = \text{Not}(\text{Not}(x) \text{ And } \text{Not}(y))$
(De Morgan)

In other words:

- Not can be realized using Nand
- And can be realized using Nand
- Or can be realized using Nand


Theorem: Any Boolean function can be realized using only Nand.

Proof : Any Boolean function can be expressed using Not, And, and Or (DNF).
Combined with the above observations, we get the theorem.

The expressive power of Nand

Theorem: Any Boolean function can be realized using only Nand.

 Conclusion: Any computer can be built from Nand gates only:



OK, so we *can* build a computer from Nand gates only.

But how can we *actually* do it?

That's what the Nand to Tetris course is all about!

Chapter 1: Boolean logic

Theory

- Basic concepts
- Boolean algebra
- Boolean functions
- Nand

Practice

- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses

Project 1

- Introduction
- Chips
- Guidelines



Chapter 1: Boolean logic

Theory

- Basic concepts
- Boolean algebra
- Boolean functions
- Nand

Practice



- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses

Project 1


- Introduction
- Chips
- Guidelines

Logic gates


➡ Elementary gates (Nand, And, Or, Not, ...)

- Composite gates (Mux, Adder, ...)


Elementary gates

 


if (a==1 and b==1)
then out=0 else out=1

 

if (a==1 and b==1)
then out=1 else out=0

 

if (a==1 or b==1)
then out=1 else out=0


 


if (in==0)
then out=1 else out=0



Why focus on these particular gates?

- Because either {Nand} or {And, Or, Not} (as well as other subsets) can be used to span any given Boolean function
- Because they have efficient hardware implementations.


Elementary gates

  

Circuit implementations:

 
 


Composite gates

 

if (a==1 and b==1 and c==1)
then out=1 else out=0

Possible implementations:

  



- This course does not deal with physical implementations (circuits, transistors, relays... that's EE, not CS)
- We focus only on logical implementations

Chapter 1: Boolean logic

Theory

- Basic concepts
- Boolean algebra
- Boolean functions
- Nand




Practice

-  Logic gates
-  HDL
 - Hardware simulation
 - Multi-bit buses

Project 1

- Introduction
- Chips
- Guidelines

Building a chip

   


```
if ((a == 0 and b == 1) or (a == 1 and b == 0))  
    sets out = 1  
else  
    sets out = 0
```

The process

- ✓ Design the chip architecture
- ✓ Specify the architecture in HDL
- ✓ Test the chip in a hardware simulator
 - Optimize the design
 - Realize the optimized design in silicon.

Design: Requirements

 

```
if ((a == 0 and b == 1) or (a == 1 and b == 0))
  sets out = 1
else
  sets out = 1
```

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Requirement

Build a chip that delivers this functionality

```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */
CHIP Xor {
  IN a, b;
  OUT out;
  PARTS:
    // Missing implementation
```

Gate Interface

Expressed as an HDL *stub file*


Design: Implementation

```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */  
CHIP Xor {  
  IN a, b;  
  OUT out;  
  PARTS:  
    // Missing implementation
```

Gate Interface

Expressed as an
HDL *stub file*


Design: Implementation

 

```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */  
CHIP Xor {  
  IN a, b;  
  OUT out;  
  PARTS:  
    // Missing implementation
```

Gate Interface
Expressed as an
HDL *stub file*

Design: Implementation

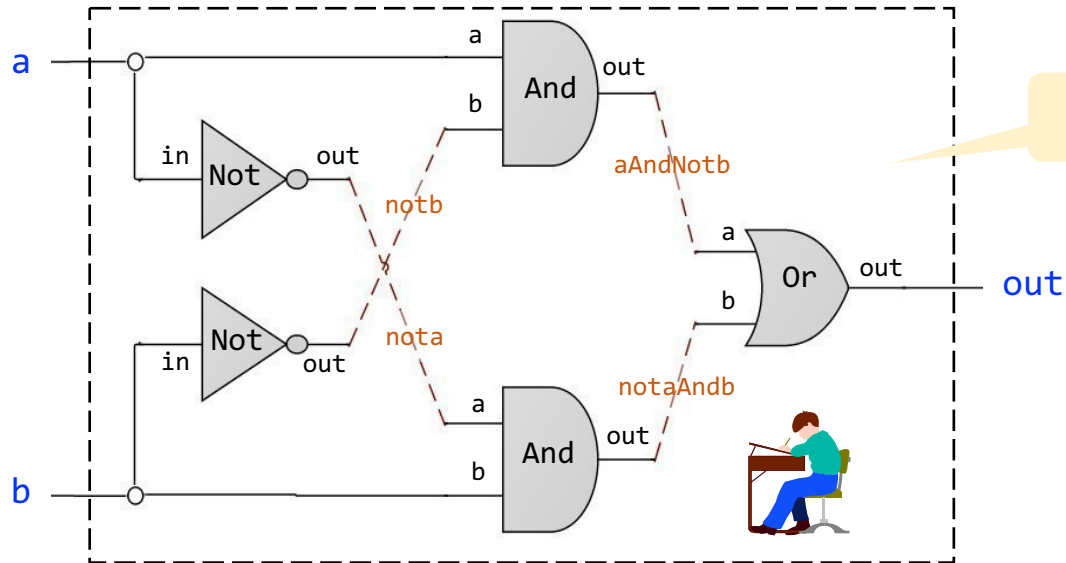


```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */  
CHIP Xor {  
  IN a, b;  
  OUT out;  
  PARTS:  
    // Missing implementation
```

Gate Interface

Expressed as an
HDL *stub file*

Design: Implementation

 

```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */
```

```
CHIP Xor {
```

```
  IN a, b;
```


```
  OUT out;
```

```
  PARTS:
```

```
    // Missing implementation
```



Design: Implementation

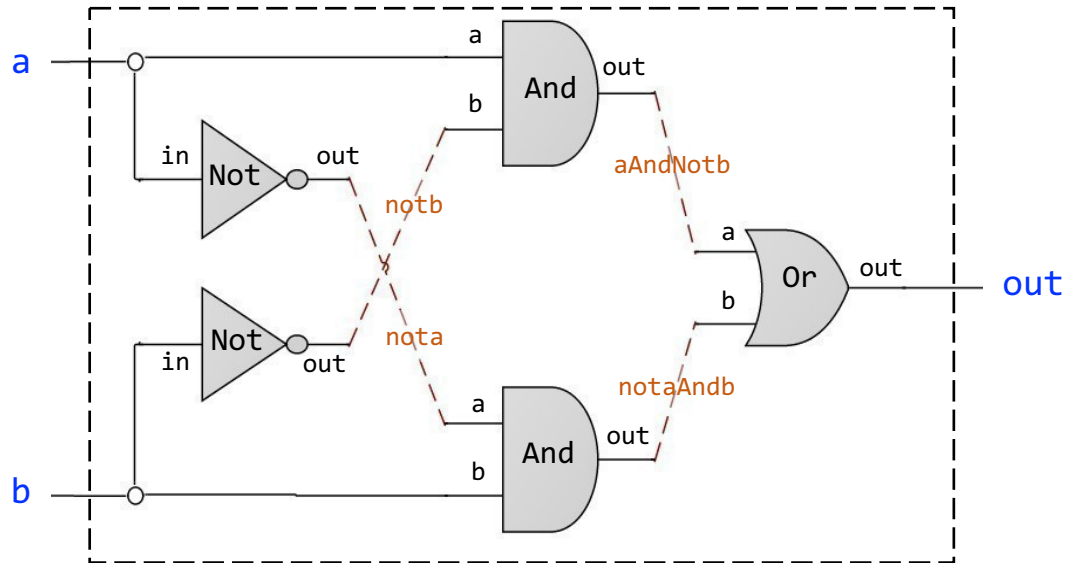

```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */
```

```
CHIP Xor {
```

```
  IN a, b;
```

```
  OUT out;
```

```
  PARTS:
```

```
    Not (in=a, out=nota);
```

```
    Not (in=b, out=notb);
```


```
    And (a=a, b=notb, out=aAndNotb);
```

```
    And (a=nota, b=b, out=notaAndb);
```

```
}
```



Design: Implementation

 


```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */  
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
  
}
```



Practice: Complete the missing HDL code

Design: Implementation

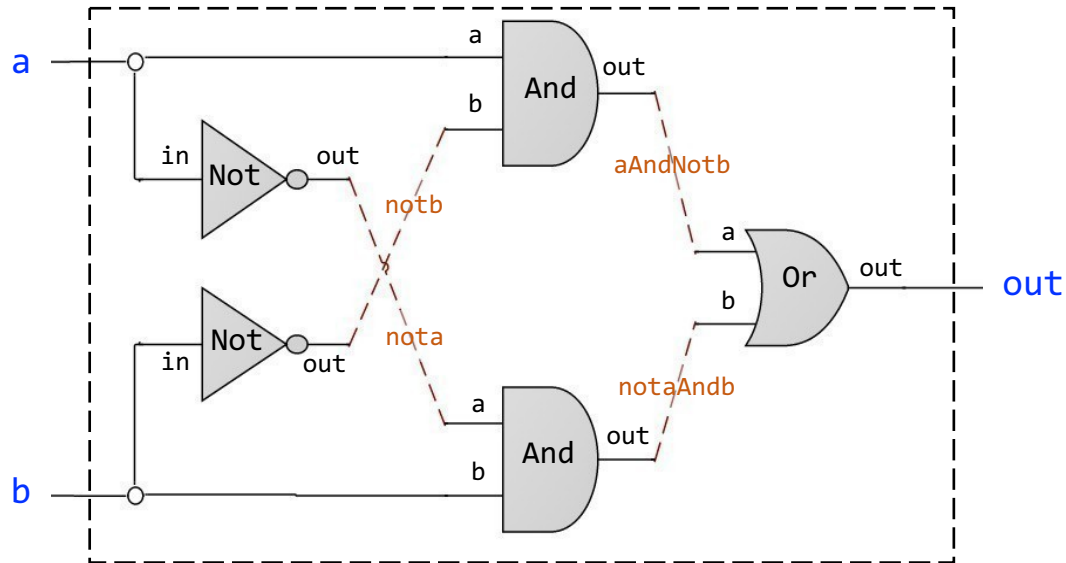

```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */
```

```
CHIP Xor {
```

```
  IN a, b;
```

```
  OUT out;
```

```
  PARTS:
```

```
    Not (in=a, out=nota);
```

```
    Not (in=b, out=notb);
```

```
    And (a=a, b=notb, out=aAndNotb);
```


```
    And (a=nota, b=b, out=notaAndb);
```

```
    Or (a=aAndNotb, b=notaAndb, out=out);
```

```
}
```



Interface / Implementation

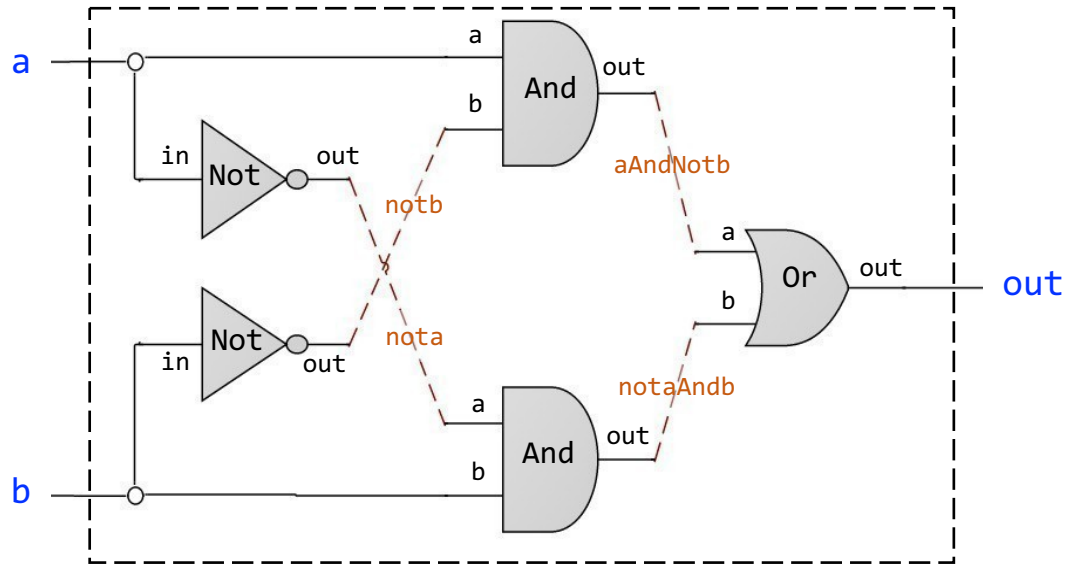

gate interface {

```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */  
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

gate Implement-ation }

A logic gate has:

- One interface
- Many possible implementations

Hardware description languages

Observations:

- HDL is a functional / declarative language
- An HDL program can be viewed as a textual specification of a chip diagram
- The order of HDL statements is insignificant.

```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */  
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

Hardware description languages

Common HDLs

- VHDL
- Verilog
- ...

Our HDL

- Similar in spirit to other HDLs
- Minimal and simple
- Provides all you need for this course

Our HDL Guide / Documentation:

[*The Elements of Computing Systems / Appendix 2: HDL*](#)




```
/** Sets out = (a And Not(b)) Or (Not(a) And b) */  
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```


Chapter 1: Boolean logic

Theory

- Basic concepts
- Boolean algebra
- Boolean functions
- Nand


Practice

-  Logic gates
-  HDL
-  Hardware simulation
 - Multi-bit buses

Project 1

- Introduction
- Chips
- Guidelines

Hardware simulation in a nutshell

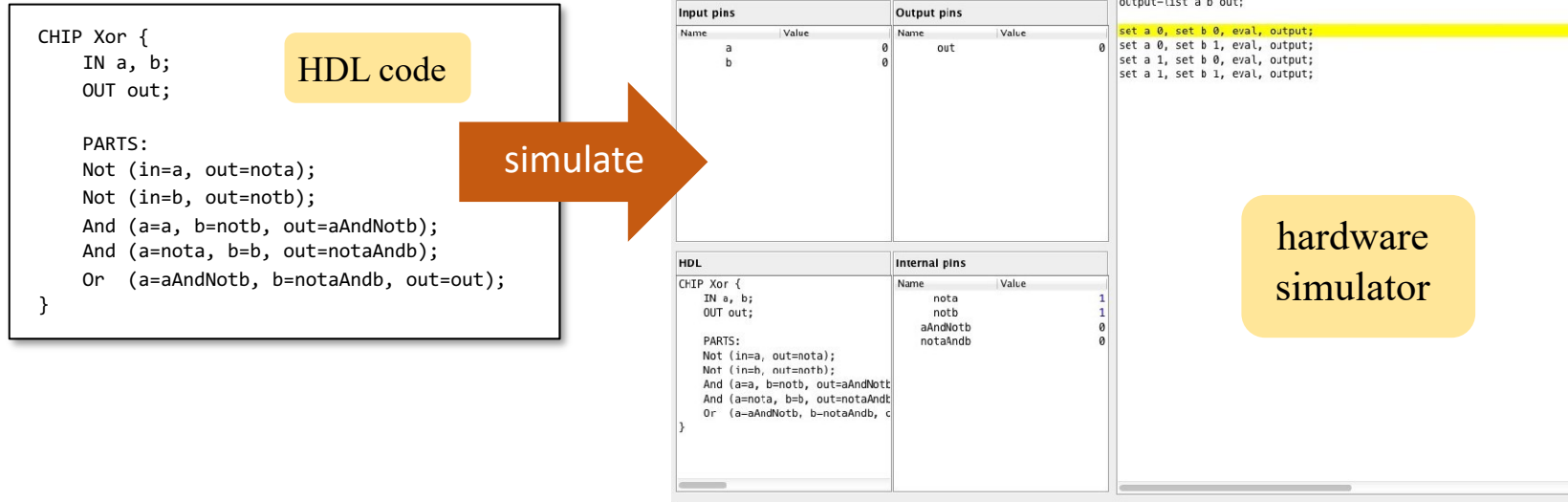

Simulation options

➡ Interactive

- Script-based.

Interactive simulation

Hardware Simulator (2.5) - /Users/shimonschocken/Desktop/nand2tetris/week 1/Xor.hdl

File View Run Help

1. Load an HDL program

3. evaluate the chip logic

2. manipulate input pins

4. inspect output pins

5. inspect internal pins

HDL code

Input pins	
Name	Value
a	0
b	1


Output pins	
Name	Value
out	1

```
CHIP Xor {
  IN a, b;
  OUT out;

  PARTS:
    Not (in=a, out=nota);
    Not (in=b, out=notb);
    And (a=a, b=notb, out=aAndNotb);
    And (a=nota, b=b, out=notaAndb);
    Or (a=aAndNotb, b=notaAndb, out=out);
}
```

Internal pins	
Name	Value
nota	1
notb	0
aAndNotb	0
notaAndb	1

Hardware simulation in a nutshell

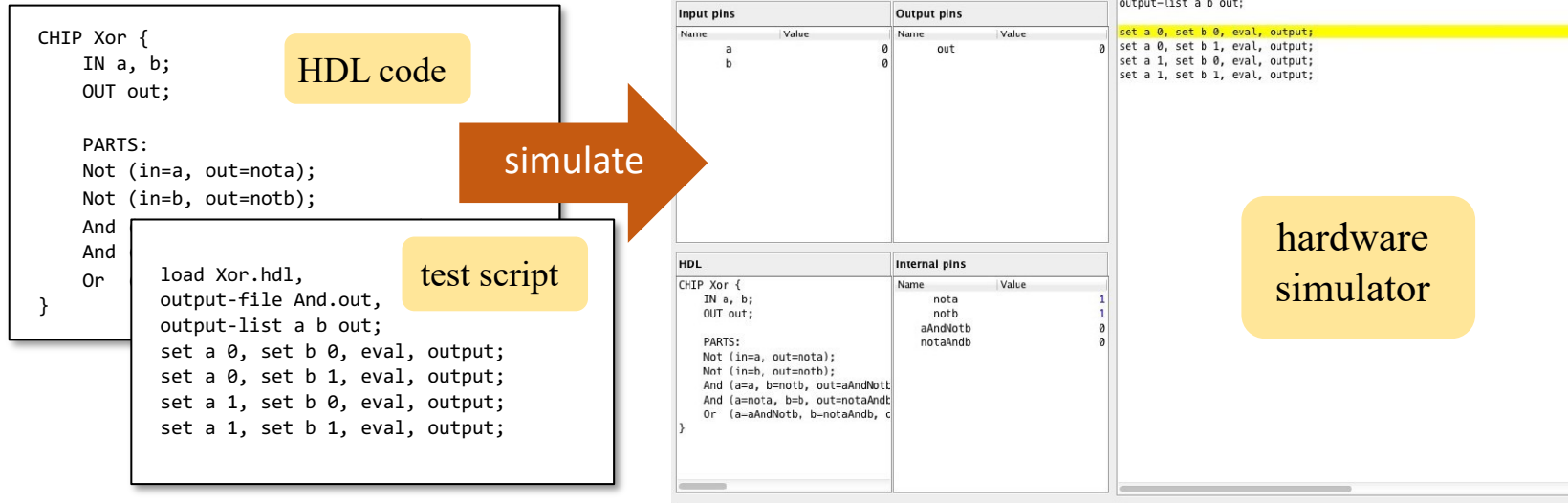

Simulation options



Interactive



Script-based.

Script-based simulation

Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

Xor.tst

```
load Xor.hdl;  
set a 0, set b 0, eval;  
set a 0, set b 1, eval;  
set a 1, set b 0, eval;  
set a 1, set b 1, eval;
```

test script = sequence of
commands to the simulator

Benefits:

- “Automatic” testing
- Replicable testing.

Script-based simulation, with an output file

Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

Xor.out

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

test
script

Output File, created
by the test script,
as a side-effect of the
simulation process

The logic of a typical test script

- Initialize:
 - ❑ Loads an HDL file
 - ❑ Creates an empty output file
 - ❑ Lists the names of the pins whose values will be written to the output file
- Repeat:
 - ❑ set – eval - output

Script-based simulation

The screenshot shows the Hardware Simulator (2.5) interface. The title bar indicates the file path: `/Users/shimonschocken/Desktop/nand2tetris/week 1/Xor.hdl`. The menu bar includes File, View, Run, and Help. The toolbar contains various icons for simulation control, with blue circles highlighting the 'Run' (double right arrow) and 'Load Script' (script icon) buttons. A yellow callout '2. run the script' points to the 'Run' button. Another yellow callout '1. Load a test script' points to the 'Load Script' button. The 'View' dropdown menu is open, showing 'Program flow', 'D...', and 'Scr...', with a yellow callout 'inspect the output file' pointing to 'Scr...'. The 'Chip Name' field is set to 'Xor' and 'Time' is 0. The 'Input pins' table has columns 'Name' and 'Value', with rows for 'a' and 'b'. The 'Output pins' table has columns 'Name' and 'Value', with a row for 'out'. The 'HDL' pane shows the chip definition for 'Xor'. The 'Internal pins' table lists internal signals and their values. The script editor on the right contains a test script. A yellow callout 'test script' points to the script. The output file 'Xor.out' is displayed as a truth table. A yellow callout 'HDL code' points to the HDL code in the HDL pane.

Hardware Simulator (2.5) - /Users/shimonschocken/Desktop/nand2tetris/week 1/Xor.hdl

File View Run Help

Chip Name: Xor Time: 0

Input pins

Name	Value
a	
b	

Output pins

Name	Value
out	

HDL

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

Internal pins

Name	Value
nota	1
notb	1
aAndNotb	0
notaAndb	0

Script Editor

```
load Xor.hdl,  
output-file Xor.out,  
output-list a b out;  
  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

View: Scr...

inspect the output file

test script

Xor.out

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

HDL code

Script-based simulation


Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

Xor.out



a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Script-based simulation, with a compare file

Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
compare-to Xor.cmp,  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

Simulation-with-compare-file logic

- When each output command is executed, the outputted line is compared to the corresponding line in the compare file
- If the two lines are not the same, the simulator throws a comparison error.

Xor.out

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Xor.cmp

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

compare

Script-based simulation, with a compare file

Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
compare-to Xor.cmp,  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

Demos:

[Experimenting with Built-In Chips](#)

[Building and Testing HDL-based Chips](#)

[Script-Based Chip Testing](#)

Xor.out

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

compare

Xor.cmp





a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Chapter 1: Boolean logic

Theory

- Basic concepts
- Boolean algebra
- Boolean functions
- Nand

Practice

-  Logic gates
-  HDL
-  Hardware simulation
-  Multi-bit buses

Project 1

- Introduction
- Chips
- Guidelines

Multi-bit bus

- Sometimes we wish to manipulate a *sequence of bits* as a single entity
- Such a multi-bit entity is termed “bus”

Example: 16-bit bus


15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
1	0	0	0	1	0	0	0	1	1	0	1	1	1	0	1

MSB = Most
significant bit

LSB = Least
significant bit

Working with buses: Example
 
```
/* Adds two 16-bit values. */  
CHIP Adder {  
  IN a[16], b[16];  
  OUT out[16];  
  
  PARTS:  
    ...  
}
```





	15	...	1	0
a:	1	...	1	1
b:	0	...	1	0
c:	0	...	0	1
out:	1	...	1	0

```
/* Adds three 16-bit inputs. */  
CHIP Adder3Way {  
  IN a[16], b[16], c[16];  
  OUT out[16];  
  
  PARTS:  
    Adder(a= , b= , out= );  
    Adder(a= , b= , out= );  
}
```

Working with buses: Example
  
```
/* Adds two 16-bit values. */  
CHIP Adder {  
  IN a[16], b[16];  
  OUT out[16];  
  
  PARTS:  
  ...  
}
```



```
/* Adds three 16-bit inputs. */  
CHIP Adder3Way {  
  IN a[16], b[16], c[16];  
  OUT out[16];  
  
  PARTS:  
    Adder(a=a, b=b, out=ab);  
    Adder(a=ab, b=c, out=out);  
}
```


n -bit value (bus) can be treated as a single entity

Creates an internal bus pin (ab)

Working with individual bits within buses

```
/* Returns 1 if a==1 and b==1,  
 * 0 otherwise. */
```
 
```
CHIP And {  
  IN a, b;  
  OUT out;  
  ...  
}
```



```
/* 4-way And: Ands 4 bits. */
```

```
CHIP And4Way {  
  IN a[4];  
  OUT out;
```

```
  PARTS:
```

```
    And(a=      , b=      , out=      );
```

```
    And(a=      , b=      , out=      );
```

```
    And(a=      , b=      , out=      );
```

```
}
```

Working with individual bits within buses

```
/* Returns 1 if a==1 and b==1,  
 * 0 otherwise. */
```

```
CHIP And {  
  IN a, b;  
  OUT out;  
  ...  
}
```

a:

3	2	1	0
0	1	1	1

out:

0

```
/* 4-way And: Ands 4 bits. */
```

```
CHIP And4Way {  
  IN a[4];  
  OUT out;
```

```
  PARTS:
```

```
    And(a=a[0], b=a[1], out=and01);
```

```
    And(a=and01, b=a[2], out=and012);
```

```
    And(a=and012, b=a[3], out=out);
```



```
}
```

Input bus pins can
be subscripted.

Working with individual bits within buses

```
/* Returns 1 if a==1 and b==1,  
 * 0 otherwise. */
```
  
```
CHIP And {  
  IN a, b;  
  OUT out;  
  ...  
}
```



```
/* 4-way And: Ands 4 bits. */
```

```
CHIP And4Way {  
  IN a[4];  
  OUT out;
```

PARTS:

```
And(a=a[0], b=a[1], out=and01);  
And(a=and01, b=a[2], out=and012);  
And(a=and012, b=a[3], out=out);
```

```
}
```

Input bus pins can
be subscripted.



```
/* Bit-wise And of two 4-bit inputs */
```

```
CHIP And4 {  
  IN a[4], b[4];  
  OUT out[4];
```

Working with individual bits within buses

```
/* Returns 1 if a==1 and b==1,  
 * 0 otherwise. */
```
  
```
CHIP And {  
  IN a, b;  
  OUT out;  
  ...  
}
```



```
/* 4-way And: Ands 4 bits. */
```

```
CHIP And4Way {  
  IN a[4];  
  OUT out;
```

PARTS:

```
And(a=a[0], b=a[1], out=and01);  
And(a=and01, b=a[2], out=and012);  
And(a=and012, b=a[3], out=out);
```

```
}
```

Input bus pins can
be subscripted.

```
/* Bit-wise And of two 4-bit inputs */
```

```
CHIP And4 {  
  IN a[4], b[4];  
  OUT out[4];
```

PARTS:



```
And(a= , b= , out= );  
And(a= , b= , out= );  
And(a= , b= , out= );  
And(a= , b= , out= );
```

```
}
```

Working with individual bits within buses

```
/* Returns 1 if a==1 and b==1,  
 * 0 otherwise. */
```
  
```
CHIP And {  
  IN a, b;  
  OUT out;  
  ...  
}
```



```
/* 4-way And: Ands 4 bits. */
```

```
CHIP And4Way {  
  IN a[4];  
  OUT out;
```

PARTS:

```
And(a=a[0], b=a[1], out=and01);  
And(a=and01, b=a[2], out=and012);  
And(a=and012, b=a[3], out=out);
```

```
}
```

Input bus pins can be subscripted.

```
/* Bit-wise And of two 4-bit inputs */
```

```
CHIP And4 {  
  IN a[4], b[4];  
  OUT out[4];
```

PARTS:

```
And(a=a[0], b=b[0], out=out[0]);  
And(a=a[1], b=b[1], out=out[1]);  
And(a=a[2], b=b[2], out=out[2]);  
And(a=a[3], b=b[3], out=out[3]);
```

```
}
```

Output bus pins can be subscripted

Chapter 1: Boolean logic

Theory

- Basic concepts
- Boolean algebra
- Boolean functions
- Nand



Practice

- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses



Project 1

- Introduction
- Chips
- Guidelines

Chapter 1: Boolean logic

Theory

- Basic concepts
- Boolean algebra
- Boolean functions
- Nand

Practice

- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses

Project 1

 Introduction

- Chips
- Guidelines

Built-in chips

We provide built-in versions of the chips built in this course (in `tools/builtInChips`).

For example:

Xor.hdl

```
/** Sets out to a Xor b */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    Not (in=a, out=nota);
    Not (in=b, out=notb);
    And (a=a, b=notb, out=aAndNotb);
    And (a=nota, b=b, out=notaAndb);
    Or (a=aAndNotb, b=notaAndb, out=out);
}
```

Implemented in HDL

Xor.hdl

```
/** Sets out to a Xor b */
CHIP Xor {
    IN a, b;
    OUT out;

    BUILTIN Xor;
    // implemented by a Xor.java class.
}
```

Implemented in Java

A built-in chip has the same interface as the regular chip, but a different implementation

Behavioral simulation

- Before building a chip in HDL, one can implement the chip logic in a high-level language
- Enables experimenting with / testing the chip abstraction before actually building it
- Enables high-level planning and testing of hardware architectures.

Demo: [Loading and testing a built-in chip in the hardware simulator](#)

Hardware construction projects

Key players:

- Architect:
 - Decides which chips are needed
 - Specifies the chips
- Developers:
 - Build / test the chips



In Nand to Tetris:

The architect is the course instructor; the developers are the students

For each chip, the architect supplies:

- Built-in chip
- Chip API (skeletal HDL program = stub file)
- Test script
- Compare file

Given these resources, the developers (students) build the chips.

The developer's view (of, say, a Xor gate)

Xor.hdl

```
/** Sets out to a Xor b */  
CHIP Xor {  
    IN a, b;  
    OUT out;  
  
    PARTS:  
        // Implementation missing  
}
```

stub
file

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
compare-to Xor.cmp  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

test
script

These files specify:

- The chip interface (.hdl)
- How the chip is supposed to behave (.cmp)
- How to test the chip (.tst)

compare
file


Xor.cmp

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0


The developer's task:

Implement the chip (complete the supplied .hdl file),
using these resources.

Nand to Tetris Roadmap: Hardware

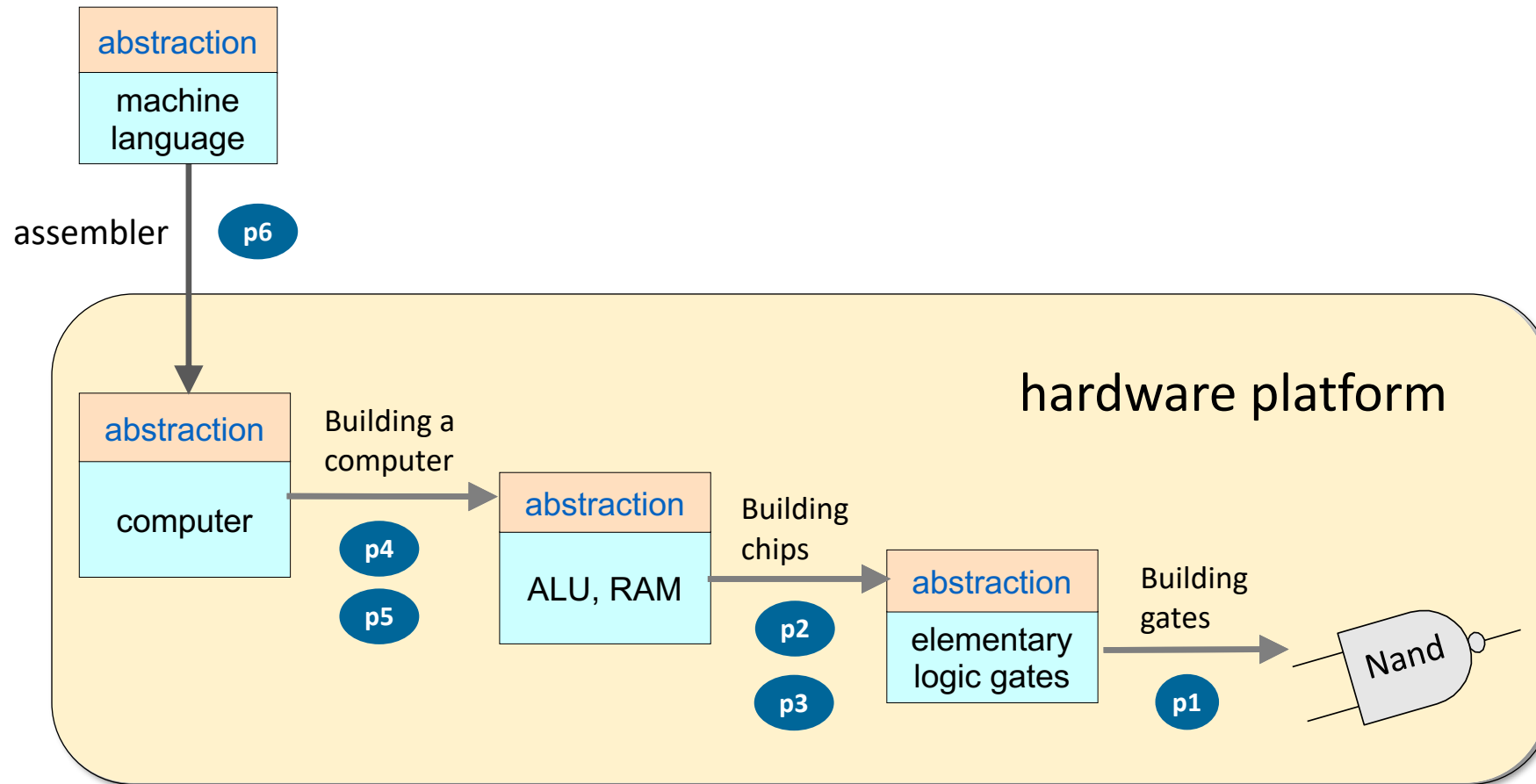

Project 1

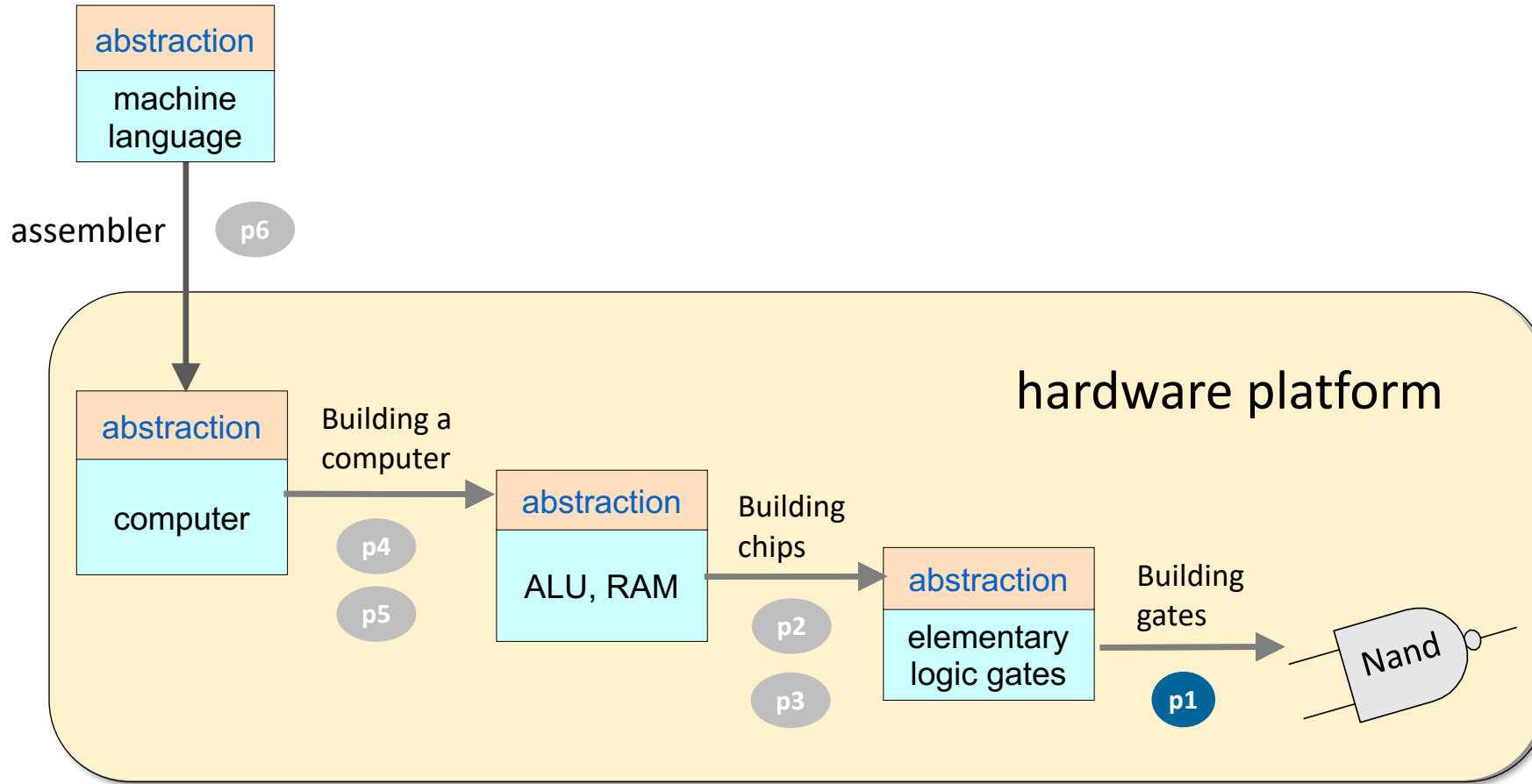

Project 1

Build 15 elementary logic gates

Project 1

Given: Nand

Goal: Build the following gates:

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux
- DMux

16-bit variants

- Not16
- And16
- Or16
- Mux16

Multi-way variants

- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way

Why these 15 particular gates?

- Commonly used gates
- Comprise all the elementary logic gates needed to build our computer.

Project 1

Given: Nand

Goal: Build the following gates:

Elementary logic gates

- Not
- And
- Or
- Xor

➡ Mux

➡ DMux


16-bit variants

- Not16
- And16
- Or16
- Mux16


Multi-way variants

- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way

Multiplexor / Demultiplexor

 
 
```
if (sel == 0)
  out = a
else
  out = b
```





```
if (sel == 0)
  {a, b} = {in, 0}
else
  {a, b} = {0, in}
```

Widely used in:

- Hardware design
- Communications networks.

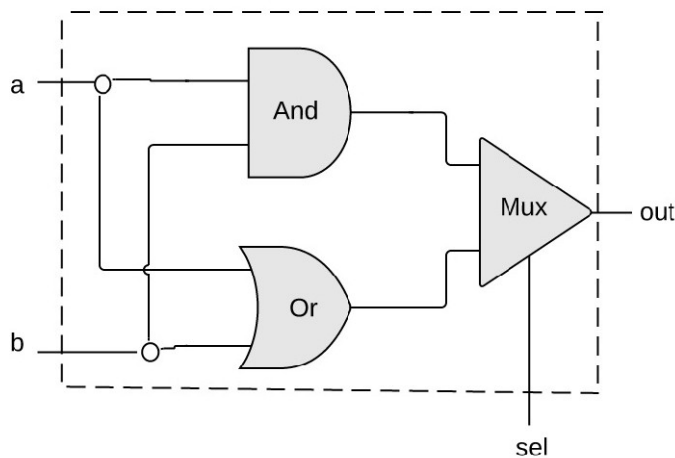 
Example 1: Using Mux logic to build a programmable gate



Mux.hdl


```
CHIP AndMuxOr {  
    IN a, b, sel;  
    OUT out;  
  
    PARTS:  
        And (a=a, b=b, out=andOut);  
        Or (a=a, b=b, out=orOut);  
        Mux (a=andOut, b=orOut, sel=sel, out=out);  
}
```

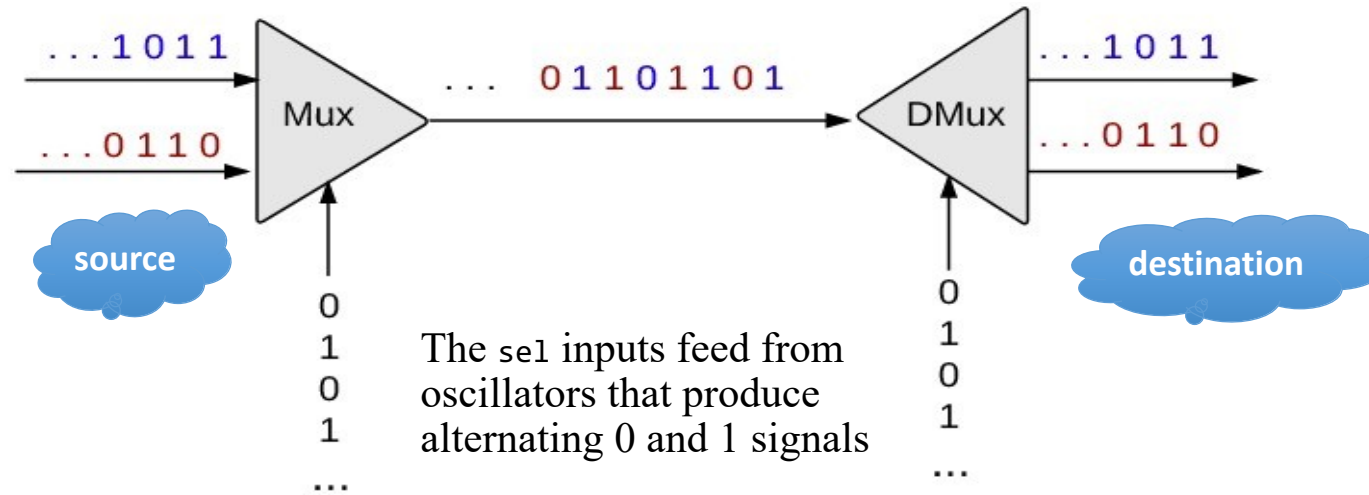Example 2: Using Mux logic in communications networks



- Enables transmitting multiple messages simultaneously using a single, shared communications line
- Unrelated to this course.

Multiplexor

 

```
if (sel == 0)
    out = a
else
    out = b
```

a	b	sel	out
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

sel	out
0	a
1	b

abbreviated
truth table

Mux.hdl


```
CHIP Mux {
    IN a, b, sel;
    OUT out;

    PARTS:
        // Put your code here:
}
```

Implementation tip

Can be implemented from the gates And, Or, Not.

Demultiplexor

 

```
if (sel == 0)
    {a, b} = {in, 0}
else
    {a, b} = {0, in}
```

in	sel	a	b
0	0	0	0
0	1	0	0
1	0	1	0
1	1	0	1

- Acts like the “inverse” of a multiplexor
- Channels the single input value into one of two possible destinations

DMux.hdl

```
CHIP DMux {
    IN in, sel;
    OUT a, b;

    PARTS:
        // Put your code here:
}
```

Implementation tip

Similar to the Mux implementation.

Project 1

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux
- DMux

16-bit variants

- Not16
- And16
- Or16
- Mux16

Multi-way variants

- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way

Project 1

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux
- DMux


16-bit variants

- Not16
- And16
- Or16
- Mux16

Multi-way variants

- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way

And16

 

Example:

a =	1	0	1	0	1	0	1	1	0	1	0	1	1	1	0	0
b =	0	0	1	0	1	1	0	1	0	0	1	0	1	0	1	0
<hr/>																
out =	0	0	1	0	1	0	0	1	0	0	0	0	1	0	0	0

```
CHIP And16 {  
  IN a[16], b[16];  
  OUT out[16];  
  
  PARTS:  
    // Put your code here:  
}
```

Implementation tip

A straightforward 16-bit extension of the elementary And gate

(See notes about working with *multi-bit buses*).

Project 1

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux
- DMux

16-bit variants

- Not16
- And16
- Or16
- Mux16

Multi-way variants

- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way

Project 1

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux
- DMux


16-bit variants

- Not16
- And16
- Or16
- Mux16

Multi-way variants

- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way

16-bit, 4-way multiplexor

 

sel[1]	sel[0]	out
0	0	a
0	1	b
1	0	c
1	1	d

Mux4Way16.hdl

```
CHIP Mux4Way16 {  
  IN a[16], b[16], c[16], d[16],  
      sel[2];  
  OUT out[16];  
  
  PARTS:  
    // Put your code here:  
}
```

Implementation tip:

Can be built from several Mux16 gates.

Chapter 1: Boolean logic

Theory

- Basic concepts
- Boolean algebra
- Boolean functions
- Nand

Practice

- Logic gates
- HDL
- Hardware simulation
- Multi-bit buses

Project 1

 Introduction

 Chips

 Guidelines

Project 1

Elementary logic gates

- ❑ Not
- ❑ And
- ❑ Or
- ❑ Xor
- ❑ Mux
- ❑ DMux

16-bit variants

- ❑ Not16
- ❑ And16
- ❑ Or16
- ❑ Mux16


Multi-way variants

- ❑ Or8Way
- ❑ Mux4Way16
- ❑ Mux8Way16
- ❑ DMux4Way
- ❑ DMux8Way



How to actually build these gates?

Files

 

```
if ((a == 0 and b == 1) or
    (a == 1 and b == 0))
    sets out = 1
else
    sets out = 0
```

Xor.cmp

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

For every chip built in the course
(using xor as an example), we supply
these three files

Xor.hdl (stub file)


```
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
        // Put your code here
}
```

Xor.tst

```
load Xor.hdl,
output-file Xor.out,
compare-to Xor.cmp,
output-list a b out;
set a 0, set b 0, eval, output;
set a 0, set b 1, eval, output;
set a 1, set b 0, eval, output;
set a 1, set b 1, eval, output;
```

Files

 

```
if ((a == 0 and b == 1) or
    (a == 1 and b == 0))
    sets out = 1
else
    sets out = 0
```

Xor.cmp

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

The contract:

When running your xor.hdl on the
supplied xor.tst,
your xor.out should be the same as
the supplied xor.cmp

Xor.hdl (stub file)

```
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
        // Put your code here
}
```

Xor.tst

```
load Xor.hdl,
output-file Xor.out,
compare-to Xor.cmp,
output-list a b out;
set a 0, set b 0, eval, output;
set a 0, set b 1, eval, output;
set a 1, set b 0, eval, output;
set a 1, set b 1, eval, output;
```

Project 1 folder

(.hdl, .tst, .cmp files):
nand2tetris/projects/01

Tools:

- Text editor
(for completing the .hdl files)
- Hardware simulator:
nand2tetris/tools

Tools

Tools

- Text editor (for completing the given .hdl stub-files)
- Hardware simulator: `nand2tetris/tools`


Guides

- [Hardware Simulator Tutorial](#)
- [HDL Guide](#)

From Nand to Tetris

Building a Modern Computer From First Principles

www.nand2tetris.org



- Home
- Projects
- Book
- Software
- Demos
- License
- Papers
- Cool Stuff
- About
- Team
- Stay in Touch
- Q&A

Project 1: Boolean Logic


Background

A typical computer architecture is based on a set of elementary logic gates like And, Or, Mux, etc., as well as their bit-wise versions And16, Or16, Mux16, etc. (assuming a 16-bit machine). This project engages you in the construction of a typical set of basic logic gates. These gates form the elementary building blocks from which more complex chips will be later constructed.

Objective

Build all the logic gates described in Chapter 1 (see list below), yielding a basic chip-set. The only building blocks that you can use in this project are primitive Nand gates and the composite gates that you will gradually build on top of them.

Chip interfaces

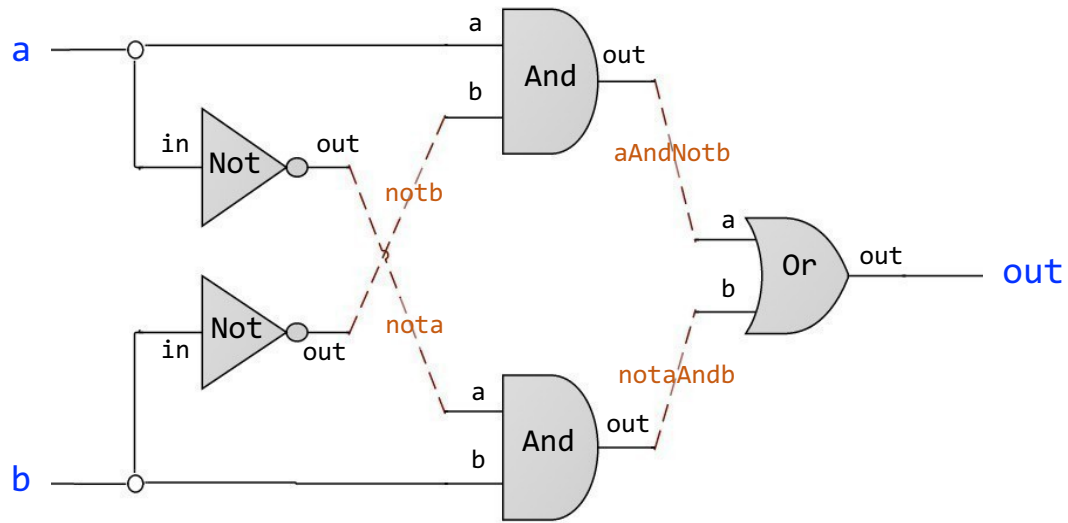

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in= , out= );  
    Not (in= , out= );  
    And (a= , b=, out=);  
    And (a= , b=, out=);  
    Or  (a= , b=, out=);  
}
```

If I want to use some chip-parts,
how do I figure out their signatures?




Chip interfaces: [Hack chip set API](#)

Open the Hack chip set API in a window, and copy-paste chip signatures into your HDL code, as needed

```
Add16 (a= ,b= ,out= );
ALU (x= ,y= ,zx= ,nx= ,zy= ,ny= ,f= ,no= ,out= ,zr= ,ng= );
And16 (a= ,b= ,out= );
And (a= ,b= ,out= );
Aregister (in= ,load= ,out= );
Bit (in= ,load= ,out= );
CPU (inM= ,instruction= ,reset= ,outM= ,writeM= ,addressM= );
DFF (in= ,out= );
DMux4Way (in= ,sel= ,a= ,b= ,c= ,d= );
DMux8Way (in= ,sel= ,a= ,b= ,c= ,d= ,e= ,f= ,g= ,h= );
Dmux (in= ,sel= ,a= ,b= );
Dregister (in= ,load= ,out= );
FullAdder (a= ,b= ,c= ,sum= ,carry= );
HalfAdder (a= ,b= ,sum= , carry= );
Inc16 (in= ,out= );
Keyboard (out= );
Memory (in= ,load= ,address= ,out= );
Mux16 (a= ,b= ,sel= ,out= );
Mux4Way16 (a= ,b= ,c= ,d= ,sel= ,out= );
Mux8Way16 (a= ,b= ,c= ,d= ,e= ,f= ,g= ,h= ,sel= ,out= );
```

```
Mux8Way (a= ,b= ,c= ,d= ,e= ,f= ,g= ,h= ,sel= ,out= );
Mux (a= ,b= ,sel= ,out= );
Nand (a= ,b= ,out= );
Not16 (in= ,out= );
Not (in= ,out= );
Or16 (a= ,b= ,out= );
Or8Way (in= ,out= );
Or (a= ,b= ,out= );
PC (in= ,load= ,inc= ,reset= ,out= );
PCLoadLogic (cinstr= ,j1= ,j2= ,j3= ,load= ,inc= );
RAM16K (in= ,load= ,address= ,out= );
RAM4K (in= ,load= ,address= ,out= );
RAM512 (in= ,load= ,address= ,out= );
RAM64 (in= ,load= ,address= ,out= );
RAM8 (in= ,load= ,address= ,out= );
Register (in= ,load= ,out= );
ROM32K (address= ,out= );
Screen (in= ,load= ,address= ,out= );
Xor (a= ,b= ,out= );
```

Built-in chips

```
CHIP Foo {  
  IN ...;  
  OUT ...;  
  
  PARTS:  
    ...  
    Bar(...)   
    ...  
}
```

Q: Suppose you want to use a chip-part before you've implemented it. How to do it?

A: The simulator features built-in implementations of all the project 1 chips

Forcing the simulator to use a built-in chip, say `Bar`:


- Typically, `Bar.hd1` will be either a given stub-file, or a file that has an incomplete implementation
- Remove, or rename, the file `Bar.hd1` from the project folder
- Whenever `Bar` will be mentioned as a chip-part in some chip definition, the simulator will fail to find `Bar.hd1` in the current folder. This will cause the simulator to invoke the built-in version of `Bar` instead.

Best practice advice

- Implement the chips in the order in which they appear in the project guidelines
- If you don't implement some chips, you can still use them as chip-parts in other chips (use their built-in implementations)
- You can invent additional, “helper chips”; However, this is not necessary. Implement and use only the chips that we specified
- In each chip definition, strive to use as few chip-parts as possible
- When defining 16-bit chips, the same chip-parts may appear many times. That's fine, use copy-paste-edit.


That's It!
Go Do Project 1!

What's next?

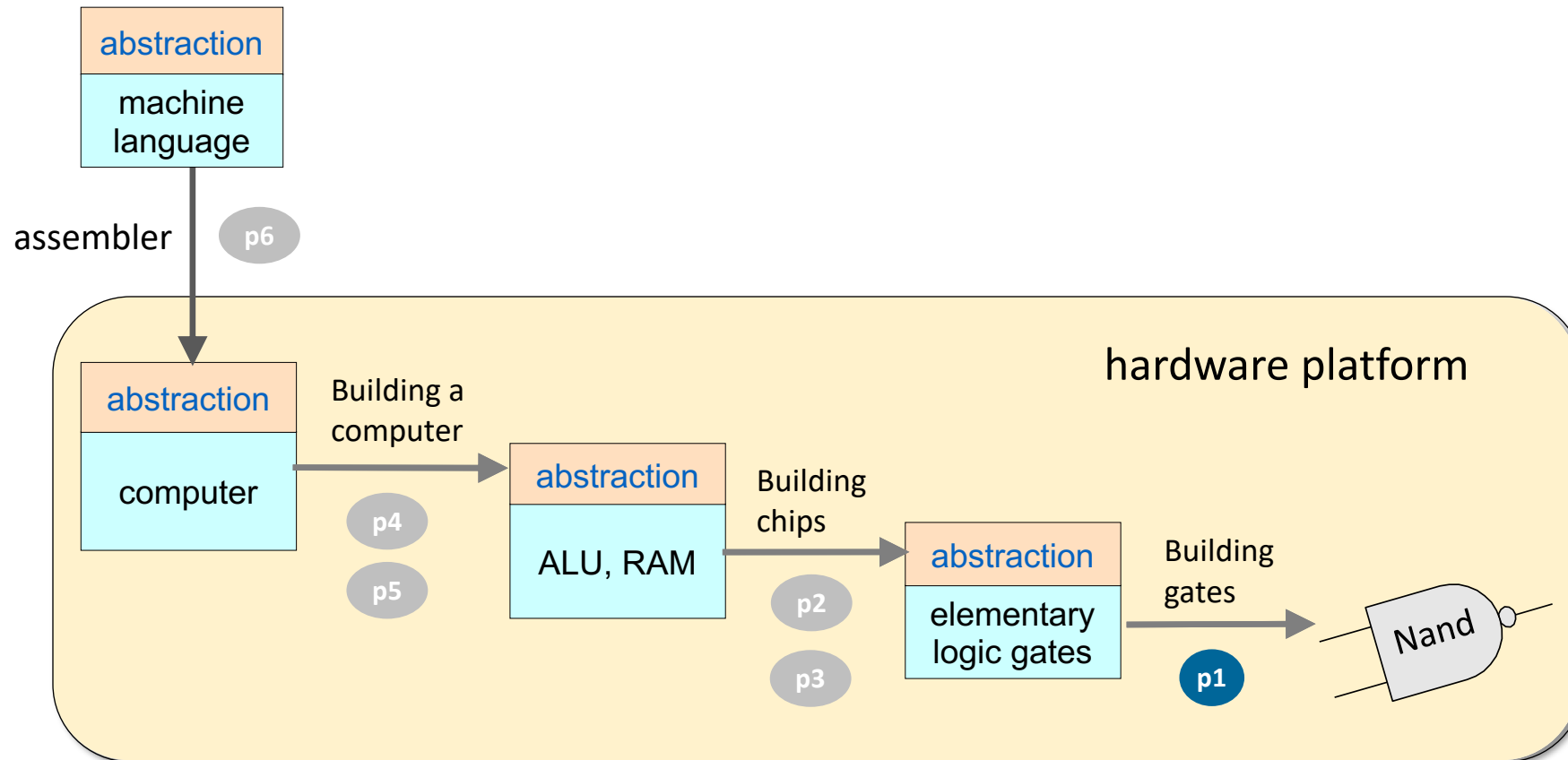

This lecture / chapter / project:
Build 15 elementary logic gates

What's next?

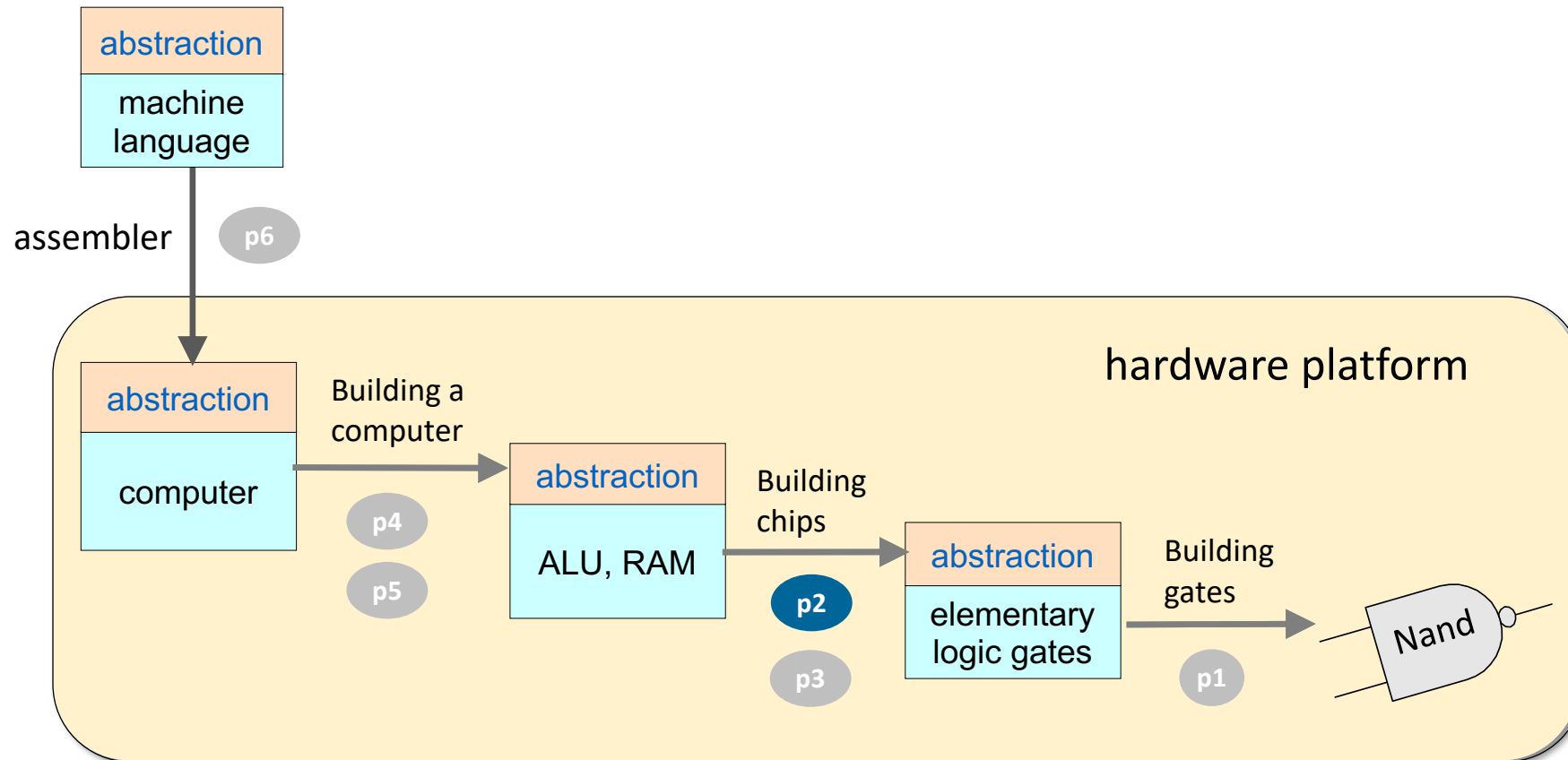

Next lecture / chapter / project:

Build chips designed to do arithmetic,
using the chips built in project 1